

Combinational Circuits


Duration: 2 hours

Section-1 (5M)

1. Design OR and XOR gate using NAND and NOR gates
2. Convert the following SOP expression to an equivalent POS expression.

$$A B C + A \bar{B} \bar{C} + A \bar{B} C + A B \bar{C} + \bar{A} \bar{B} C$$

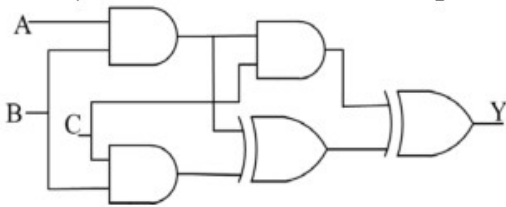
3. The output of the combinational circuit given below is



4. From the truth table below, determine the standard SOP expression.


Inputs			Output
A	B	C	X
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	0
1	0	1	0
1	1	0	1
1	1	1	0

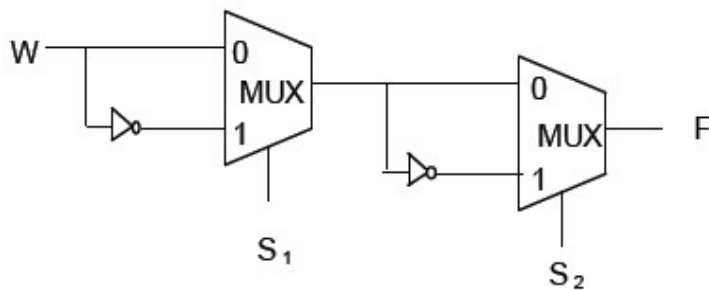5. Prove that $(A+B'+AB)(A+B')(A')=0$
6. Consider the multiplexer based logic circuit shown in the figure.



What is the Boolean function is realized by the circuit

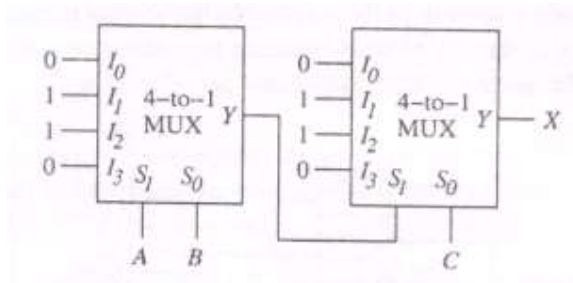7. Design the 3-bit input circuit which identifies 3 multiples?
8. In the following circuit, X is given by



9. Perform Hex addition


1. 39a+4fd
2. adf+bec

Section-2 (10M)

10. Construct a 5-to-32-line decoder using four 3-8-line decoders with enable inputs and a 2-to-4-line decoder.

11. Design and implement 4:16 decoder using 2:4 decoders only

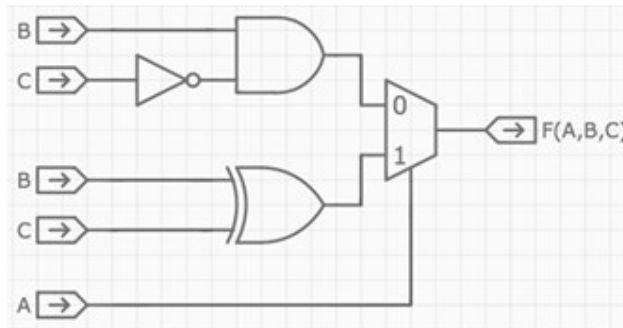12. A intern at Intel has designed the combinational circuit shown.



A	B	C	F(A,B,C)
0	0	0	
0	0	1	
0	1	0	
0	1	1	
1	0	0	
1	0	1	
1	1	0	
1	1	1	

Please fill in the truth table for F(A,B,C).

13. Design a circuit for 5-bit Fibonacci series.

