 


SEQUENTIAL ASSIGNMENT 1

1. Assuming that all flip-flops are in reset condition initially, the count sequence observed at Q_A in the circuit shown is



2. (a) Difference between latch and flip flop

(b) What is the difference between asynchronous counter and synchronous counter?

3. I) A bidirectional 4-bit shift register is storing the nibble 1110. Its input is LOW. The nibble 0111 is waiting to be entered on the serial data-input line. After two clock pulses, the shift register is storing


- a) 1110 b) 0111 c) 1000 d) 1001

1001



II) Assume there is a mod6 up counter, current state is 101. After 17 clock pulses, what is the state?

100

 

4. What does the triangle on the clock input of a $J-K$ flip-flop mean?


a. Level enabled

b. Edge-triggered

EDGE TRIGGERED



 5. A gated S-R latch and its associated waveforms are shown below. What, if anything, is wrong and what could be causing the problem?



The Q output is always low; the circuit is defective.

6. How many Flip Flops are required to make Mod 32 Bit Counter?

a. 4

b. 45

c. 3

d. 5

5

